

Name: Ezgi

Surname: Demir

ID: 22103304

Date: 03.03.2024

# EE313-Electronic Circuit Design

## Lab2 Preliminary

### Low-Dropout Voltage Regulator

## Preliminary Work

In this lab, we will focus on designing a Low-Dropout Voltage Regulator. A Low-Dropout Voltage Regulator (LDO) is a type of voltage regulator used in electronic circuits to provide a stable output voltage from a varying input voltage while minimizing the voltage drop between the input and output.

### 1) Finding $\beta$ of the pnp Transistor

In this lab we're working with BD136 pnp transistor. First, I design a very simple circuit to observe  $\beta$  of the pnp transistor (Figure 1.1). To do that with trial and error, changing the voltage and resistances I reached a linear region of the transistor, with the help of the cursor I checked  $V_c$ ,  $V_e$ ,  $V_b$  values then made sure that my transistor is not saturated (Figure 1.2 and 1.3). Then, with the formula below (Eq. 1) I derive the  $\beta$  ( $I_c$  stands for collector current and  $I_b$  stands for base current of the BJT) :

$$I_c = \beta I_b \quad (\text{eq. 1})$$

In order to check whether bjt is in its linear region,  $V_{ce}$  and  $V_{be}$  values should satisfy below values based on the pnp model :

$$V_{be} \approx -0.7 \text{ Volts}$$

$$V_{ce} \approx 0.2 \text{ Volts}$$

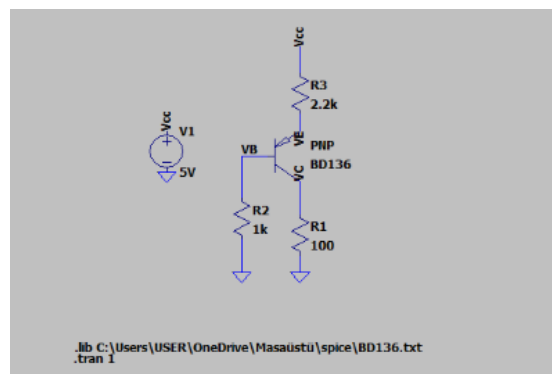


Figure 1.1 : pnp Transistor Circuit

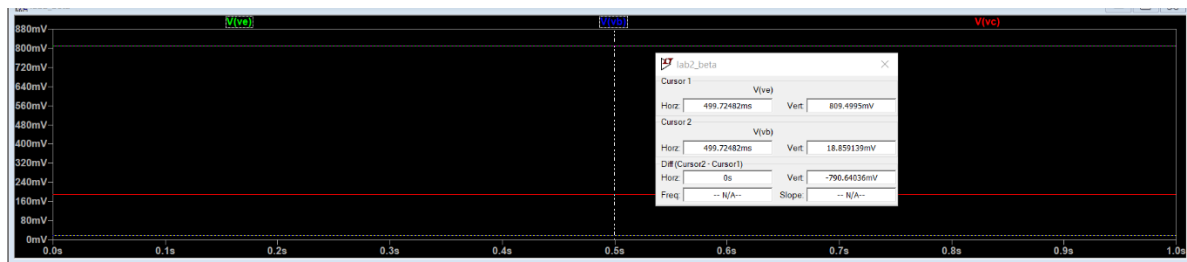


Figure 1.2 :  $V_{be} = -0.79V$  calculated ( $\approx 0.7V$ )

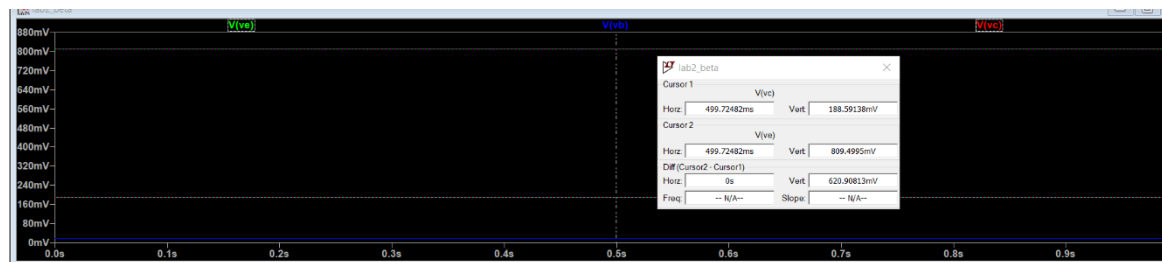


Figure 1.3 :  $V_{ce} = 620.91mV$  calculated ( $> 0.2$ )

After making sure that we are in the linear region, we check the ratio between  $I_b$  and  $I_c$  ( $\beta$ ):

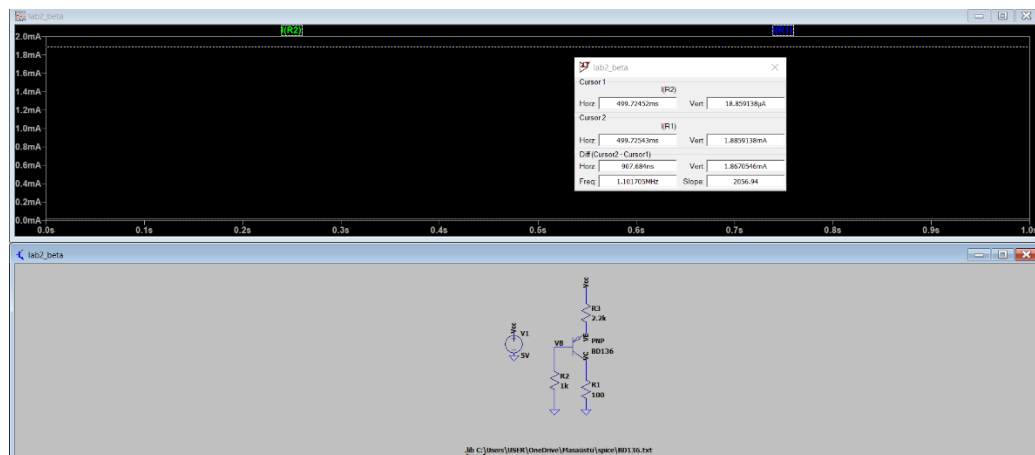


Figure 1.4 :  $I_c = 18.86\mu A$ ,  $I_b = 1.886 mA$

$$I_c = \beta I_b$$

$$18.86 \mu A = 100 \times 1.886 mA$$

$$\beta = 100$$

## 2) Designing a Low-Dropout Voltage Regulator

Lowdropout (0.7V max) voltage regulator with an output current of 100mA. A green LED should turn on if the regulator output is good. Use a power pnp BJT (BD136) to regulate the voltage, an OPAMP (LM358) to provide the feedback and a Zener diode as the voltage reference. Select an output voltage of 7V, 8V, 9V, 10V, 11V, or 12V.

Initially, I picked a zener diode voltage available in the lab which is 8.2V (BZX84C8V2L). I selected output voltage as between 11 and 12V.

### Specification:

1. Line regulation: When  $V_{in}$  is between  $V_{out}+0.7$  to  $V_{out}+6$ , the output voltage,  $V_{out}$ , changes by no more than 10mV when the output current is 20mA ( $R_L = V_{out}/0.02$ ).

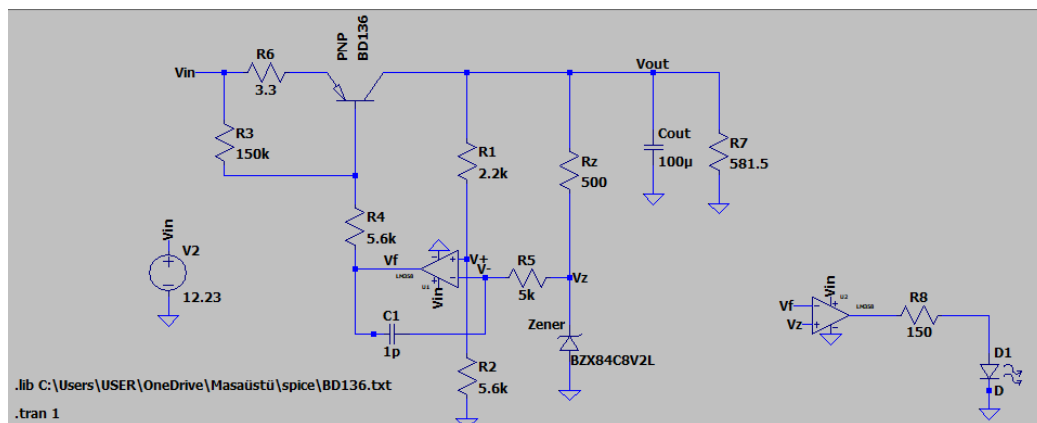


Figure 2.1 : Circuit of Specification 1

- As seen here,  $V_{in} = V_{out} + 0.6$ ,  $V_{out}$  changes by no more than 10mV when the output current is 20mA.
- Also  $R_L = R_7$  is selected from  $R_L = V_{out}/0.02 \gg 11.629738/0.02 \approx 581.5\Omega$  (However, in experimental this value will be probably 560Ω)

$V_f$  is not 0V, about 9.77V ( $V_f < V_{in} - 2V$ ), so our opamp is working in its linear region, so we can continue our design:

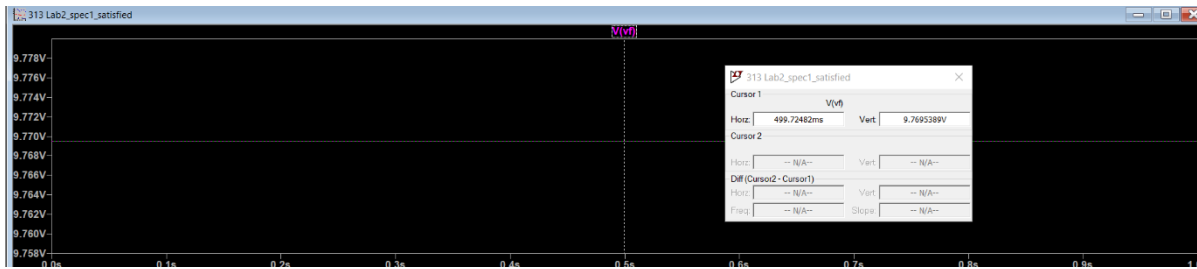


Figure 2.2 :  $9.77V (V_f < V_{in} - 2V)$ ,  $9.77V < 10.33$

$V_{out}$  doesn't change more than 10mV as seen via cursors when  $V_{in} = V_{out} + 0.6$  and  $V_{in} = V_{out} + 0.7$ :

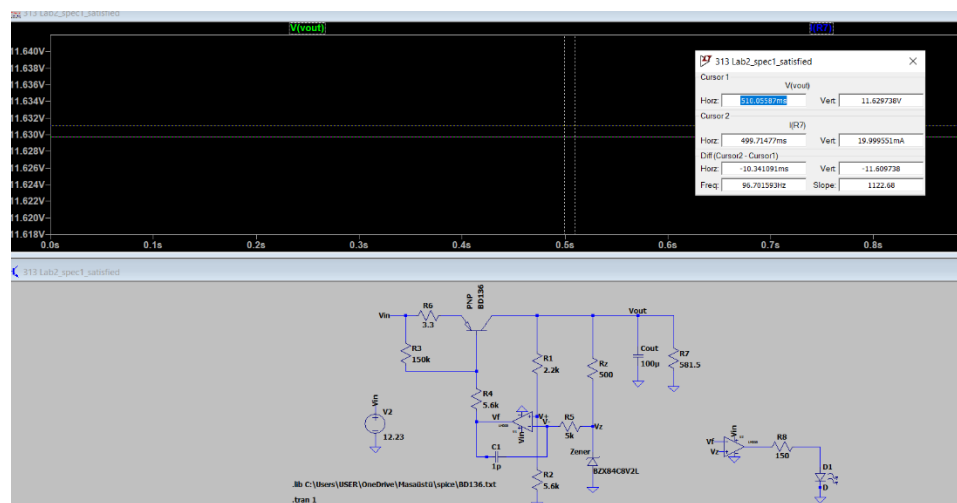


Figure 2.3 :  $V_{out} = 11.62974V$  in both cases when  $V_{in}$  is 12.33V and  $V_{in} = 12.23V$ ,  $I_{out} = 19.99955mA$

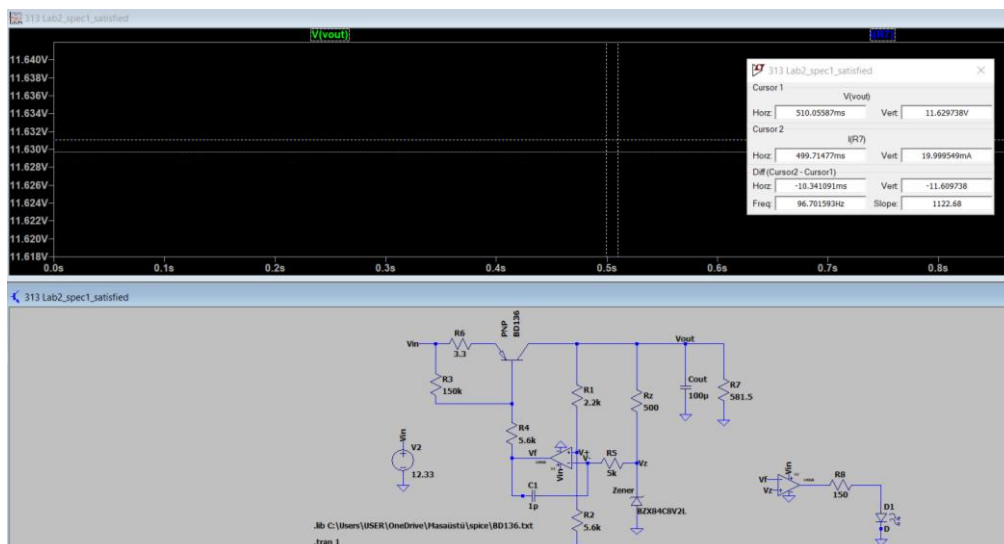


Figure 2.4:  $V_{in} = 12.33$ ,  $I_{out} = 19.99955mA$

How to decide resistors R1 and R2:

From the formula below Vout value is derived:

$$V_{out} = V_z \frac{R_1 + R_2}{R_2}$$

$$8.3492V \times \frac{(5.6k + 2.2k)}{5.6k} \approx 11.62924V$$

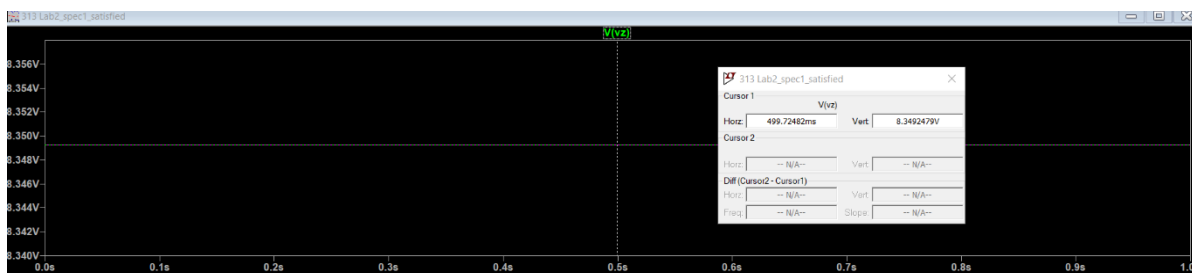


Figure 2.5 : Vzener= 8.3492V , Vout= 11.6297

### Specification:

2. Load regulation: When  $V_{in} = V_{out} + 2$ , the output voltage,  $V_{out}$ , changes no more than 50mV when

the output current changes between 5mA and 100mA ( $R_L$  is varied between  $V_{out}/0.005$  to  $V_{out}/0.1$ ).

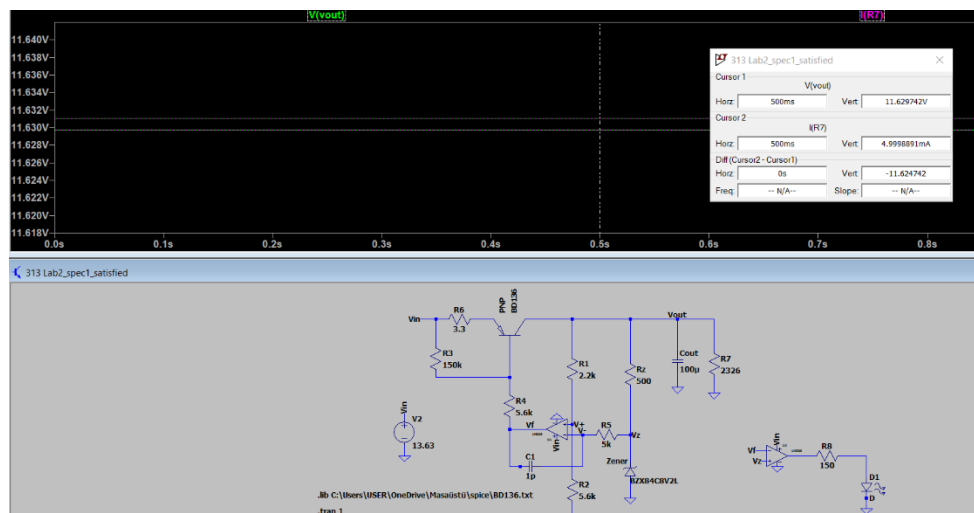


Figure 3.1 : Circuit of Specification 2,  $V_{in} = V_{out} + 2 = 13.63$  when  $R_L = V_{out}/0.005 = 2.3k$   $I_{out} = 4.99mA$

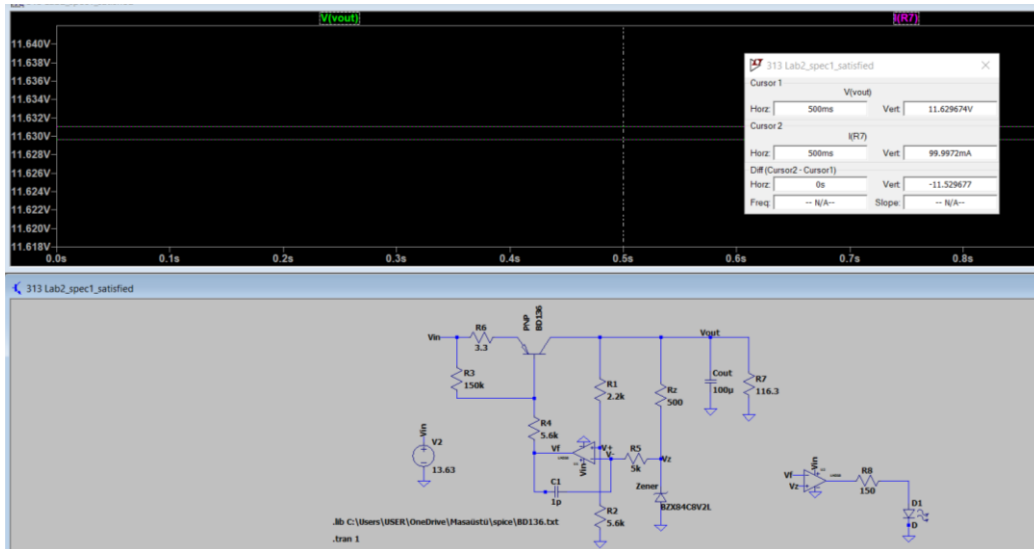


Figure 3.2 :  $V_{in}=V_{out}+2 = 13.63$  when  $R_L = V_{out}/0.1 = 116.3$ ,  $I_{out}=99.997mA$

- Also  $R_L = R_7$  is selected from  $R_L = V_{out}/0.1 = 116.3\Omega$  (However, in the experimental this value will be probably 100Ω or 120Ω, this is just for lowering the software error).

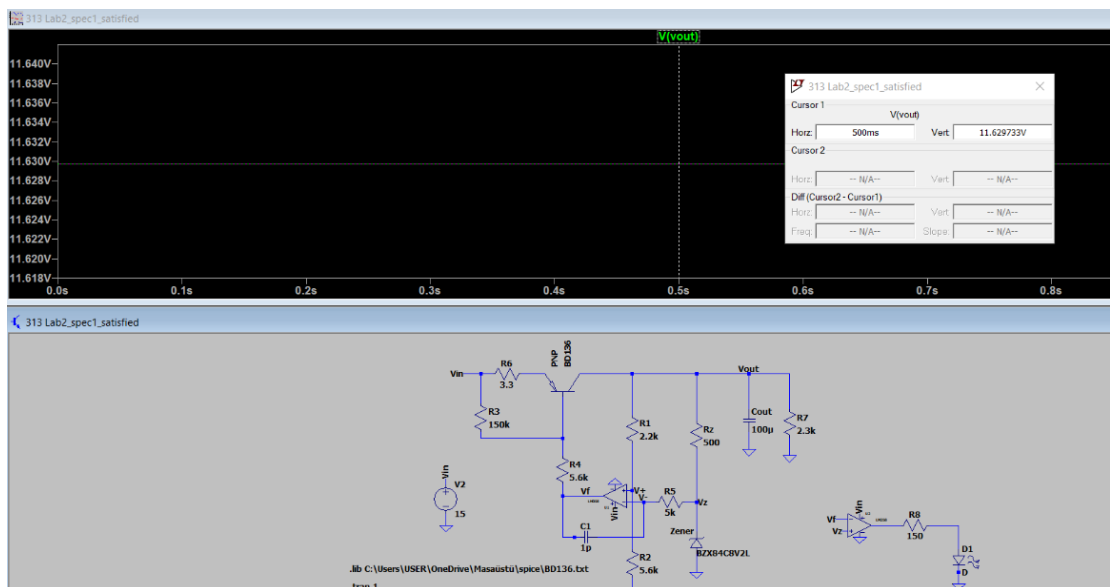


Figure 3.3 :  $V_{in}=15V$  when  $R_L = V_{out}/0.005 = 2.3k$ ,  $V_{out} = 11.629733V$

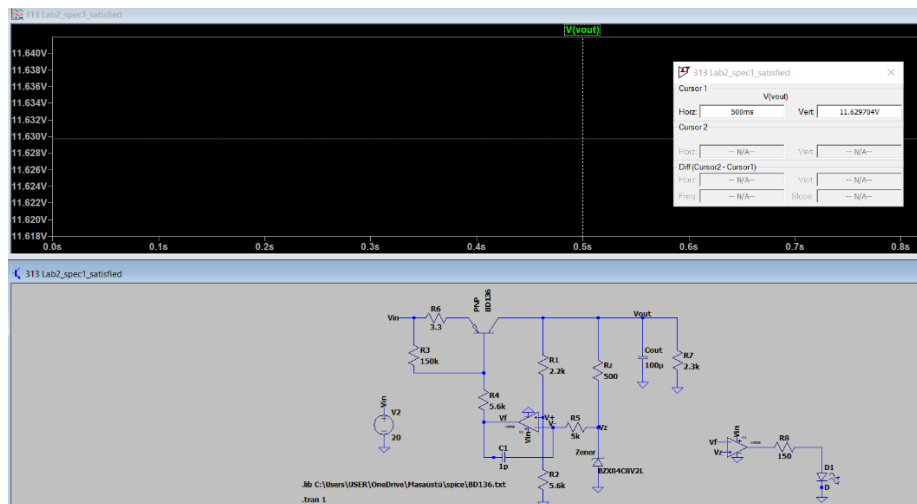


Figure 3.4 :  $V_{in}=20V$  when  $R_L = V_{out}/0.005 = 2.3k\Omega$ ,  $V_{out} = 11.629704V$

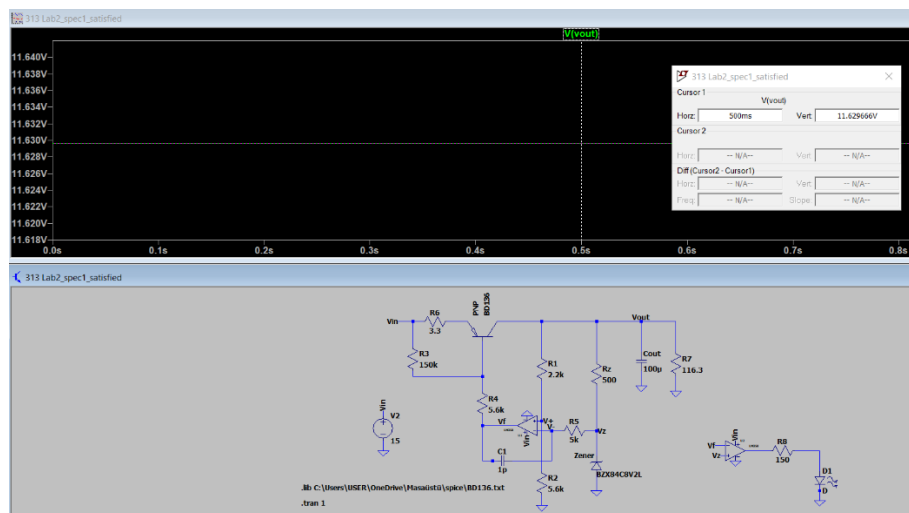


Figure 3.5 :  $V_{in}=15V$  when  $R_L = V_{out}/0.1 = 116.3\Omega$ ,  $V_{out} = 11.629666V$

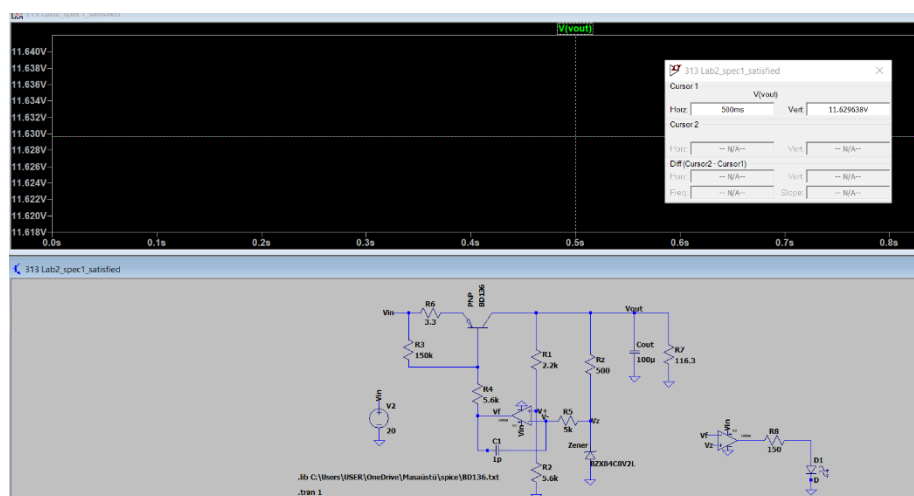


Figure 3.6 :  $V_{in}=20V$  when  $R_L = V_{out}/0.1 = 116.3\Omega$ ,  $V_{out} = 11.629638V$



### Specification:

3. An output short circuit current of smaller than 250mA when  $V_{in}=V_{out}+0.7$

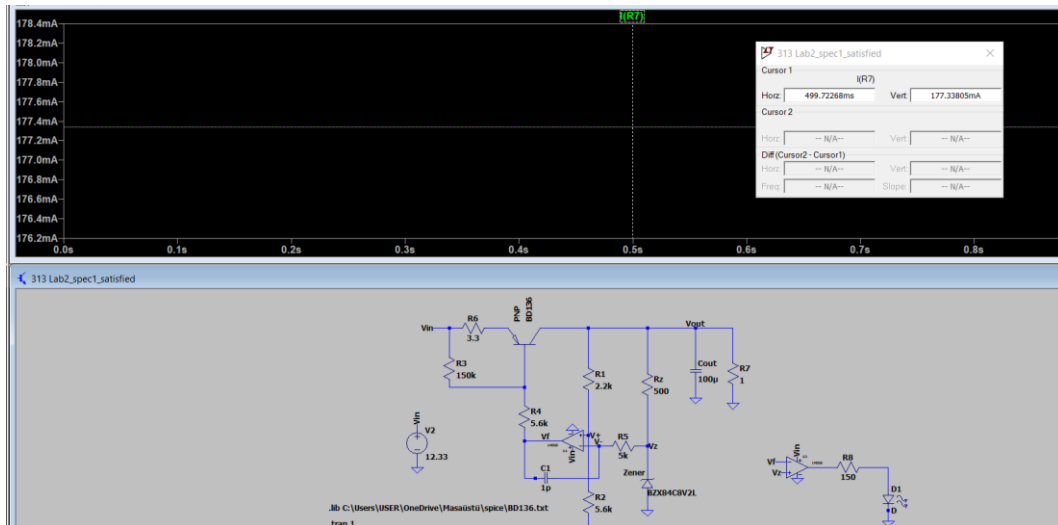


Figure 4 :  $I_{out} \approx 177.34mA$

### Specification:

4. A green LED should turn on if the regulation is achieved. Otherwise, it should turn off, for example, because the input voltage is too low or the output current is too high.

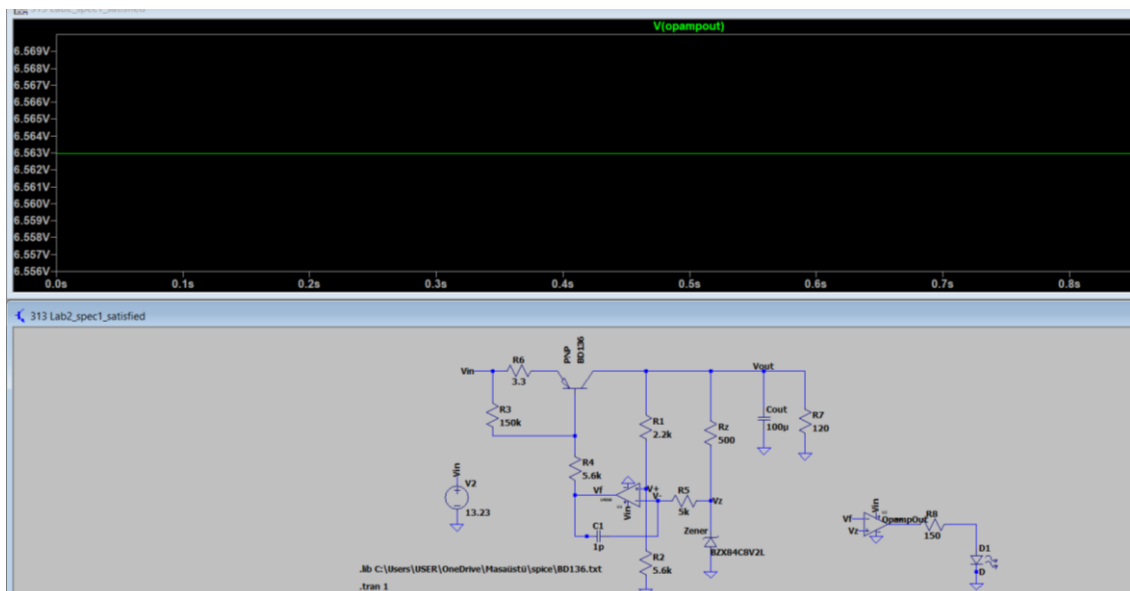


Figure 5.1 : The output of the last opamp is approximately 6.56V, so LED is ON, as we know LED turns on 1.7V

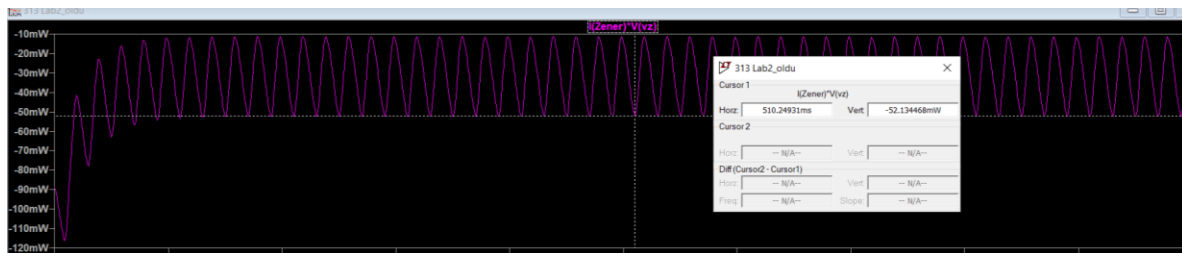


Figure 5.2 : Zener won't dissipates more than 100mW as expected, dissipates 52mW

## Thermal Analysis

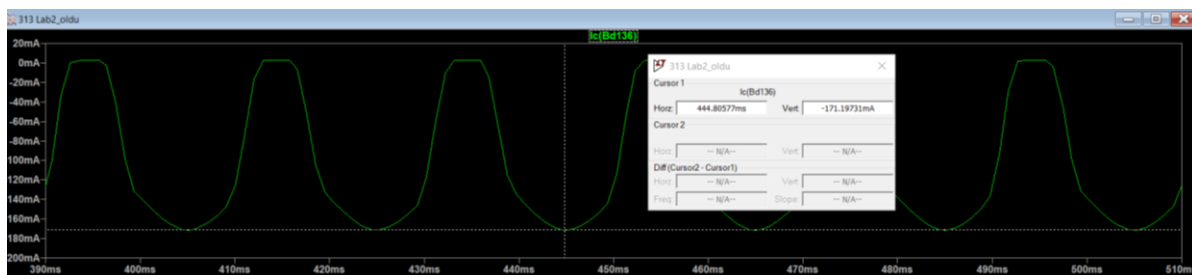


Figure 6.1 :  $I_c = 171\text{mA}$  measured

VCE calculated from the difference  $V_c$  and  $V_e = V_{ce} = 2.53\text{V}$

$$\begin{aligned}
 & T_J - T_A = R_{\theta JA} \cdot P_D \\
 & \quad \quad \quad \uparrow 25^\circ\text{C} \quad \quad \quad \uparrow 12.5 \\
 & \quad \quad \quad \downarrow 100 \\
 & T_J = 12.5 + 12.5 \\
 & T_J = 12.5 \\
 & R_{\theta JA} = R_{\theta JC} + R_{\theta AS} \\
 & 100 = 10 + 90 \\
 & T_C - T_A = R_{\theta AS} \cdot P_A \\
 & T_C - 25 = 90 \cdot \text{bmu } 614 \\
 & \quad \quad \quad \text{bmu } 101! \\
 & T_C = 64.12 \\
 & P_D = I_C V_{CE} + I_B V_{BE} \approx I_C V_{CE} \\
 & \quad \quad \quad \downarrow 2.53\text{V} \\
 & 171.8 = 434.654\text{ mW}
 \end{aligned}$$

Figure 6.2 :  $P_D = 434.65\text{ mW}$  measured, therefore  $T_c$  is about  $64^\circ\text{C}$

#	Name	RefDes	Value
1	CAP100	C1	1p
2	CAP250RP	Cout	100u
3	LED	D	
4	BD136	PNP	
5	CFR25SJR-52-100K	R1, R2, R3, R4, R5, R6, R7, R8, Rz	2.2k, 5.6k, 150k, 5.6k, 5k, 3.3, 1116.3, 150, 500
6	LM358N	U1, U2	LM358
7	BZX84C8V2LT1G	Zener	8.2V

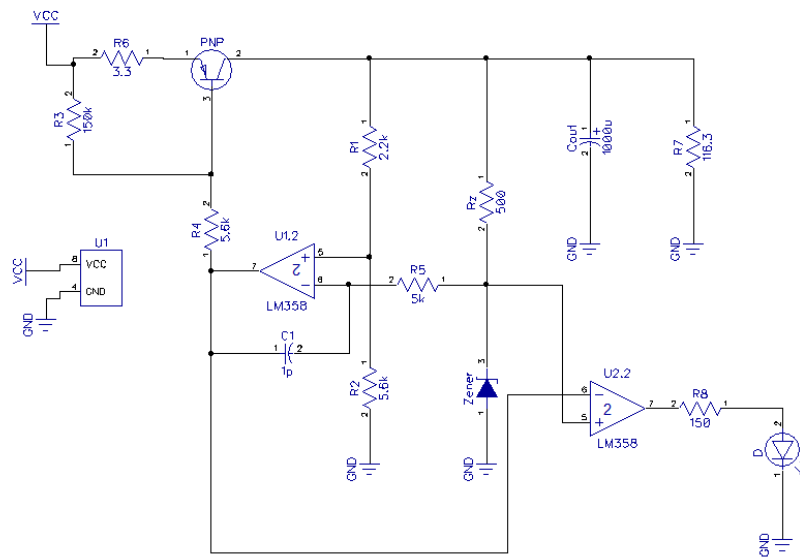


Figure 7: Diptrace Schematic and Component List

Note: The reason why I misunderstood some concepts of this lab, I needed to change my preliminary lab report. So, I submitted my report after the experimental session again!!

## REFERENCES:

- <https://www.desmos.com/scientific>
- [https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/77721/mod\\_resource/content/1/LDOAnalysis.pdf](https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/77721/mod_resource/content/1/LDOAnalysis.pdf)
- [https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/82714/mod\\_resource/content/2/HintsForLab2.pdf](https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/82714/mod_resource/content/2/HintsForLab2.pdf)
- [https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/81407/mod\\_resource/content/1/ZenerDiodeList.txt](https://moodle.bilkent.edu.tr/2023-2024-spring/pluginfile.php/81407/mod_resource/content/1/ZenerDiodeList.txt)
- Data sheet of BD146